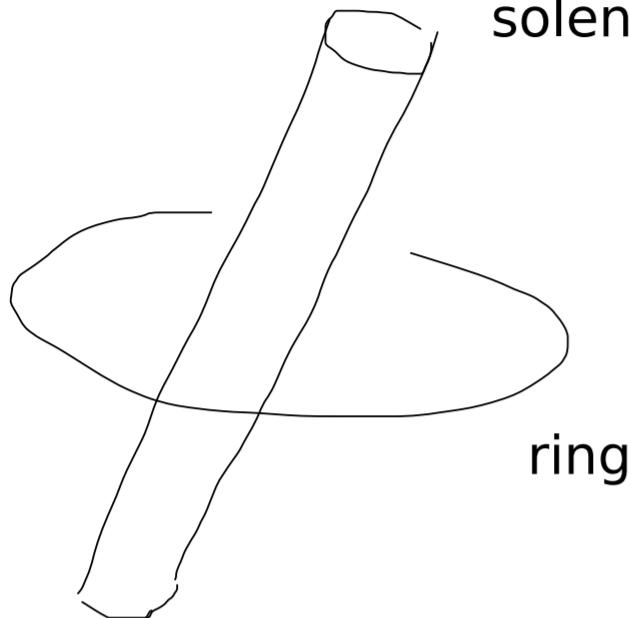


04/08/2011


$$\text{mutual inductance} \quad \phi = M I$$

examples



area

turn density

A

n

1. current in solenoid, flux through the ring

$$B = \mu_0 n I$$

$$\phi = B A = \mu_0 n A I$$

$$M = \mu_0 n A$$

what if the solinoid is tilted?

## 2. current in the ring, flux through the solinoid

ring makes the magnetic field.

$$\vec{B}(\vec{r})$$

take a piece of solinoid of length  $dr$



this piece has  $n dr$  turns.


the flux through these turns is

$$\begin{aligned} d\Phi &= \vec{B} \cdot \vec{A} n dr = \\ &= \vec{B} \cdot \vec{A} dr A n \end{aligned}$$

the total flux through the solinoid is

$$\Phi = A n \int \vec{B} \cdot \vec{A} dr = \mu_0 n A I$$

$$[M = \mu_0 n A]$$

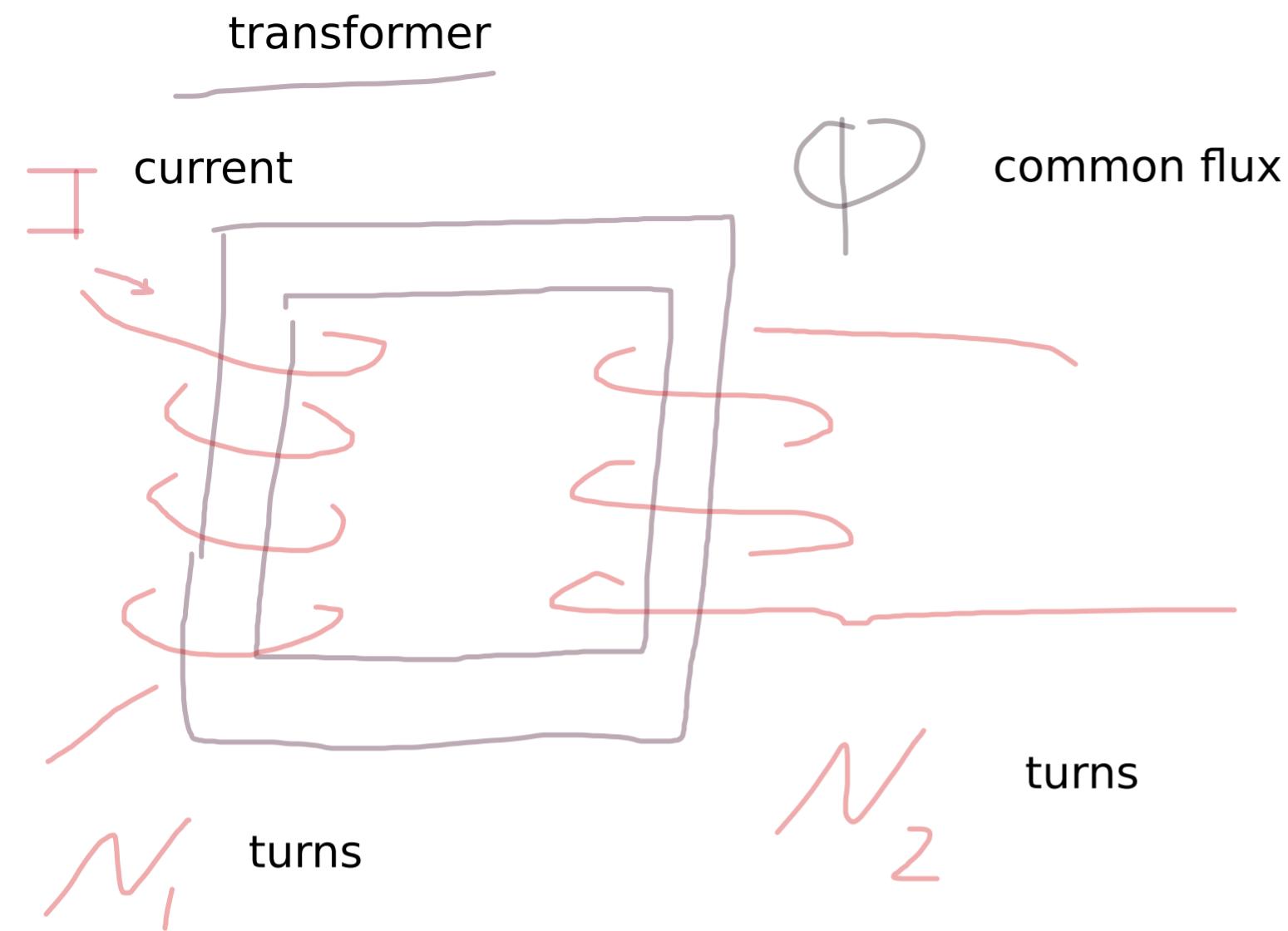

$$\Phi_1 = N_1 \phi$$

$$\Phi_2 = N_2 \phi$$

$$\begin{aligned}
 V_1 &= N_1 \frac{d\phi}{dt} = \frac{N_1}{N_2} N_2 \frac{d\phi}{dt} = \\
 &= \frac{N_1}{N_2} V_2
 \end{aligned}$$

$$\frac{V_1}{N_1} = \frac{V_2}{N_2}$$

$$P = I_1 V_1 = I_2 V_2$$


$$I_1 N_1 = I_2 N_2$$

for AC current only!!!



The end!

# Self-inductance 04/11/2011

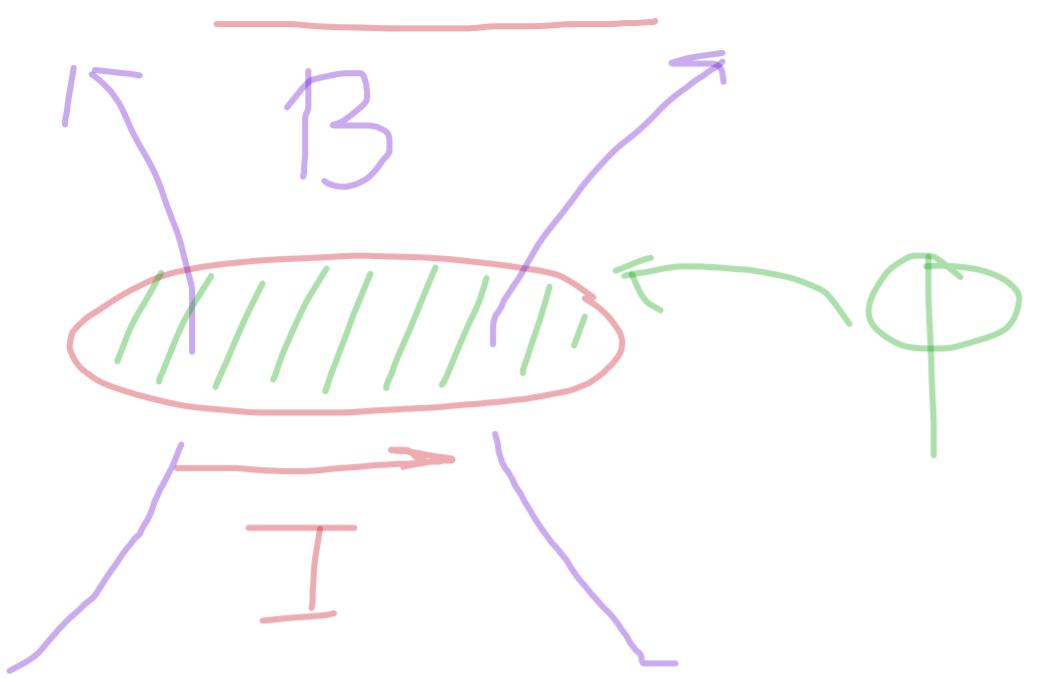


$$\Phi \sim I$$

$$\Phi = LI$$

$\uparrow$


self inductance

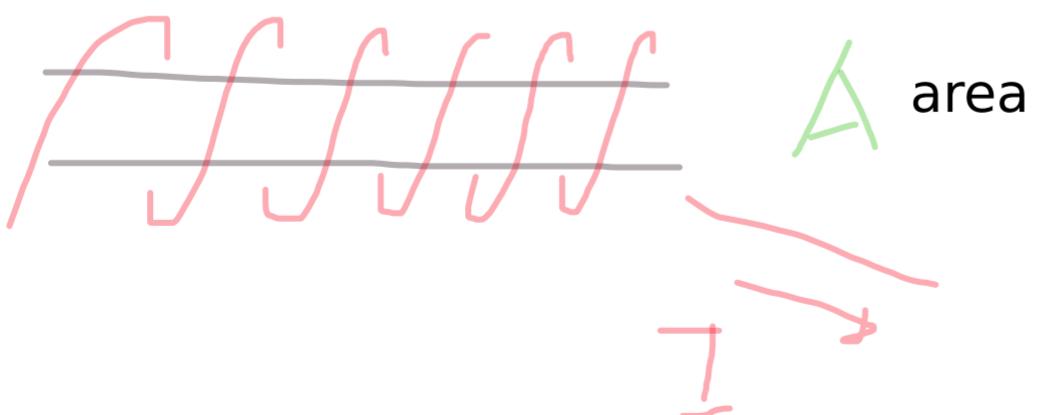

$$\Phi = N B A = n \ell \mu_0 n A I$$

$$L = n^2 A \ell \mu_0$$

for any inductor

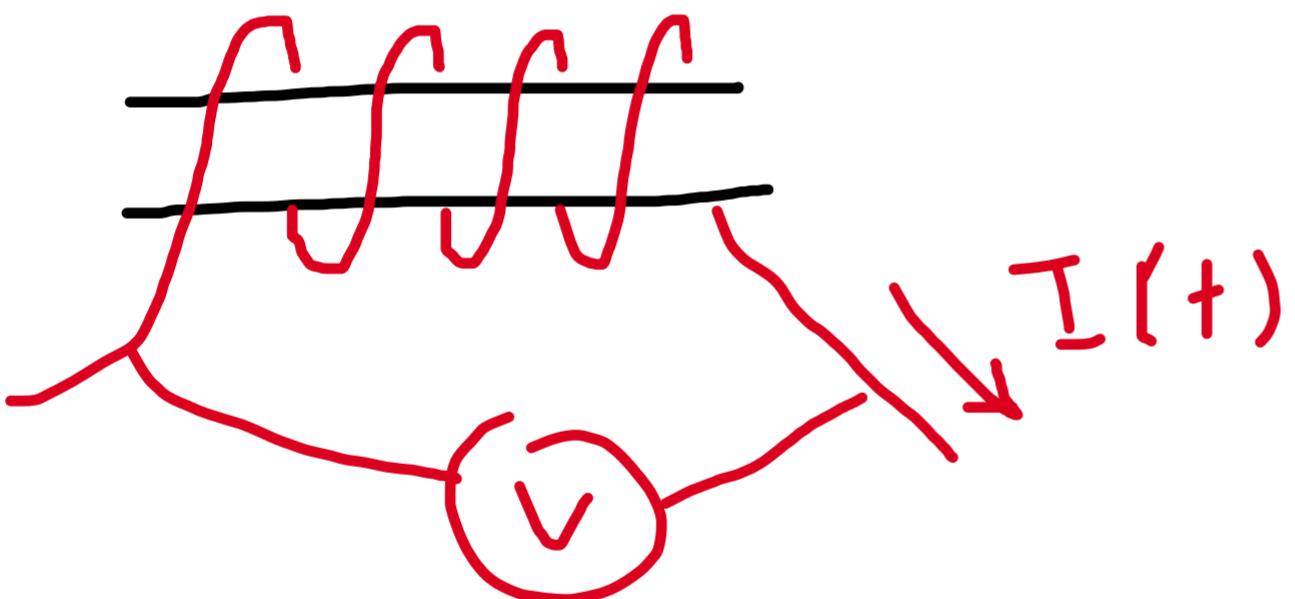


$$V = -\frac{\Delta \Phi}{\Delta t} = -L \frac{\Delta I}{\Delta t}$$

# energy of an inductor

1. increase  $I$  induces  $V$
2.  $V$  counteracts.

It takes work to increase  $I$ .

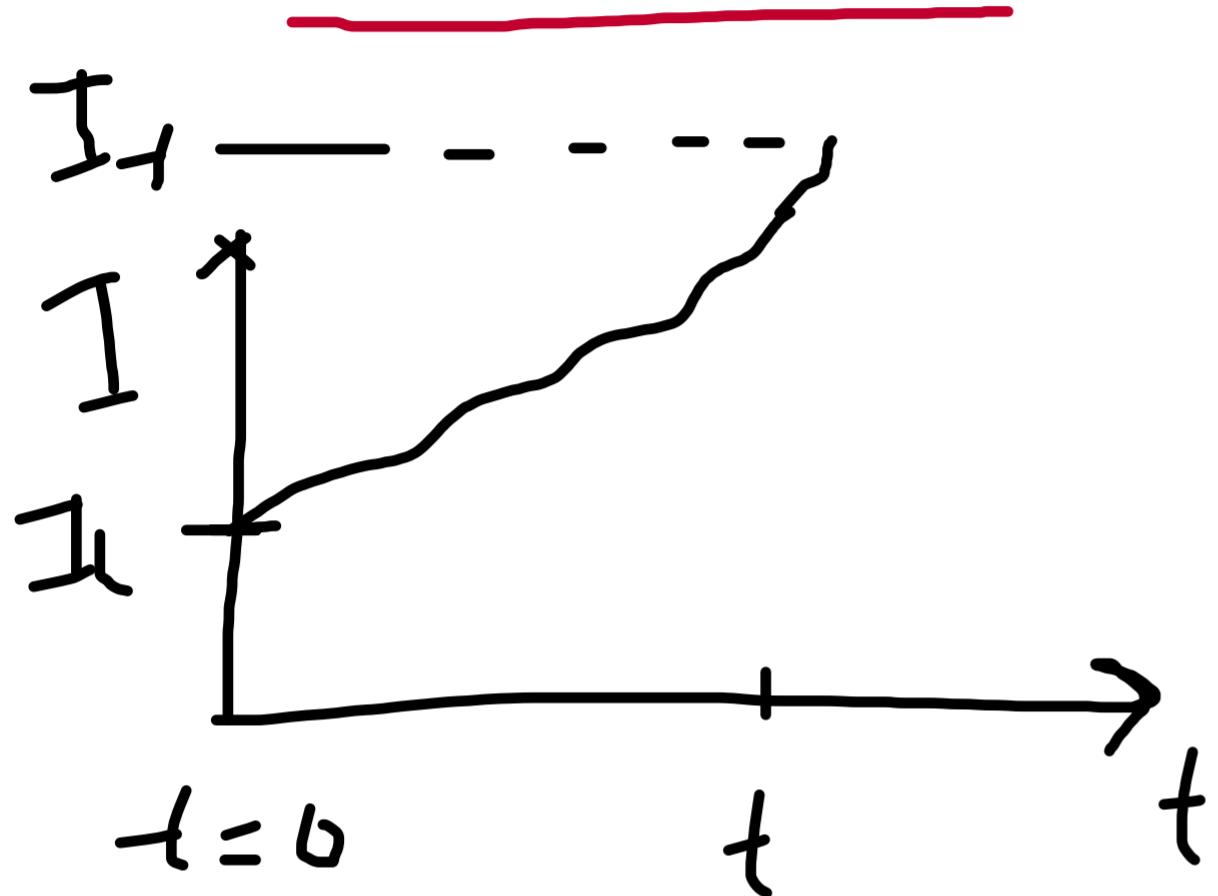

increase current from  $I$  to  $I+dI$  during time  $dt$

$$V = -L \frac{dI}{dt}$$

$$P = IV = LI \frac{dI}{dt}$$

$$W = \int_{t_1}^{t_2} P \, dt = \int_{t_1}^{t_2} L I \frac{dI}{dt} \, dt =$$

$$= \int_{I_1}^{I_2} L I dI = \frac{LI_2^2}{2} - \frac{LI_1^2}{2}$$

$$E_L = \frac{LI^2}{2}$$

Any inductor

for a solenoid

$$L = n^2 A l \mu_0$$


$$B = \mu_0 I n$$


$$E = \frac{LI^2}{2} = \frac{n^2 \mu_0 I^2}{2} l A =$$

$$= \frac{B^2}{2\mu_0} V \quad \text{Volume}$$

$$\epsilon_B = \frac{B^2}{2\mu_0}$$

energy density of magnetic field

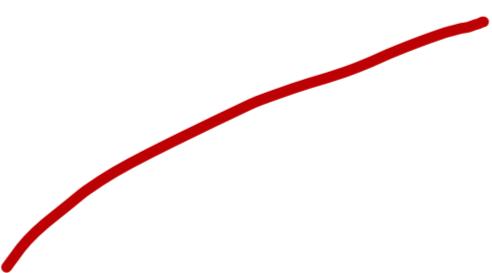

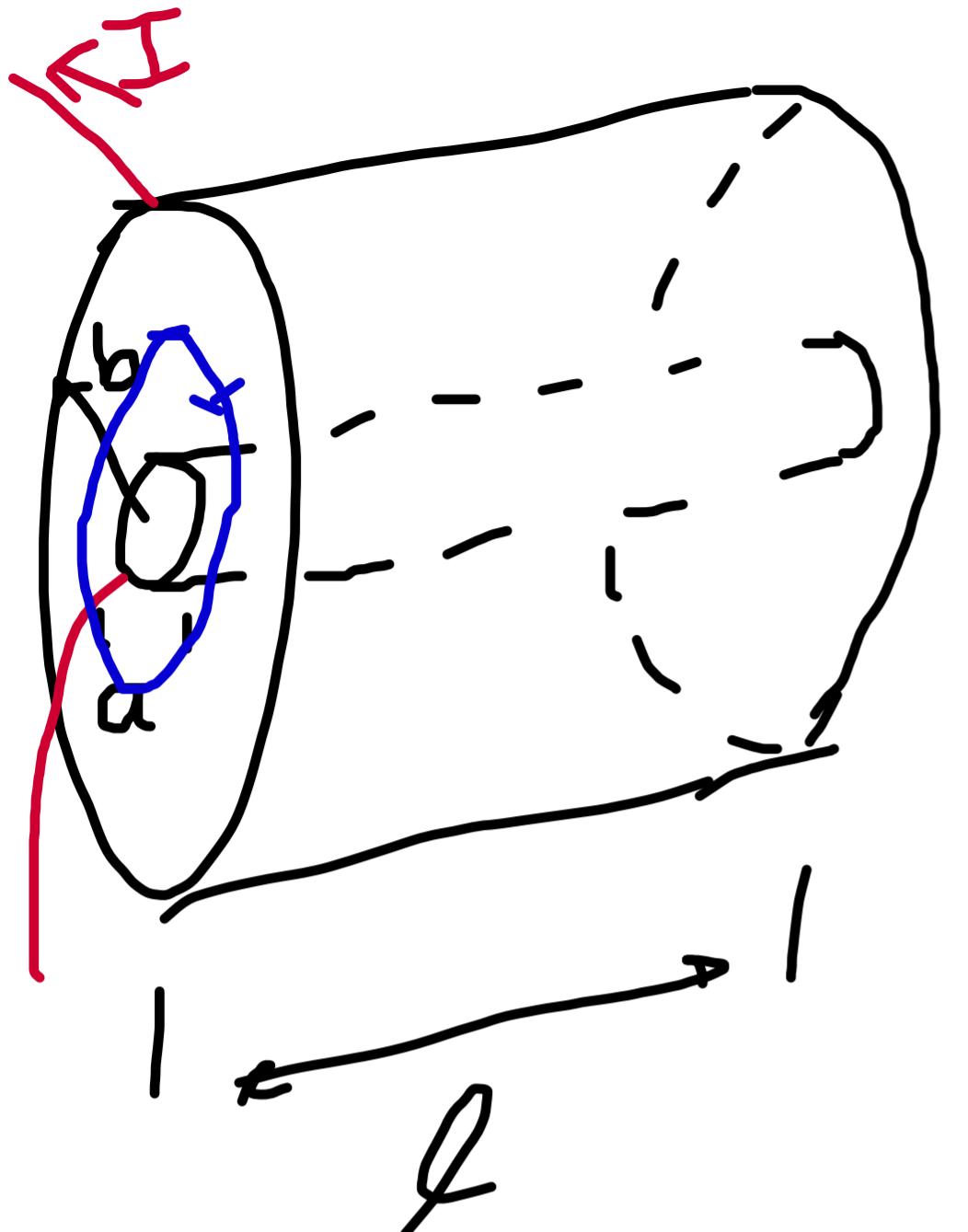

What  
is  $\angle$ ?

$$B 2\pi r = \mu_0 I$$

$$B = \frac{\mu_0 I}{2\pi} \frac{1}{r}$$

$$E = \int \frac{B^2}{2\mu_0} dV =$$

$$= \frac{\mu_0 I^2}{4\pi^2} \frac{1}{2\mu_0} \int \frac{1}{r^2} dxdydz$$



$$= \frac{\mu_0 I^2}{4\pi^2} \ln b/0c$$

$$L = \frac{\mu_0 l}{2\pi} \ln b/0c$$

The End !

# Plan

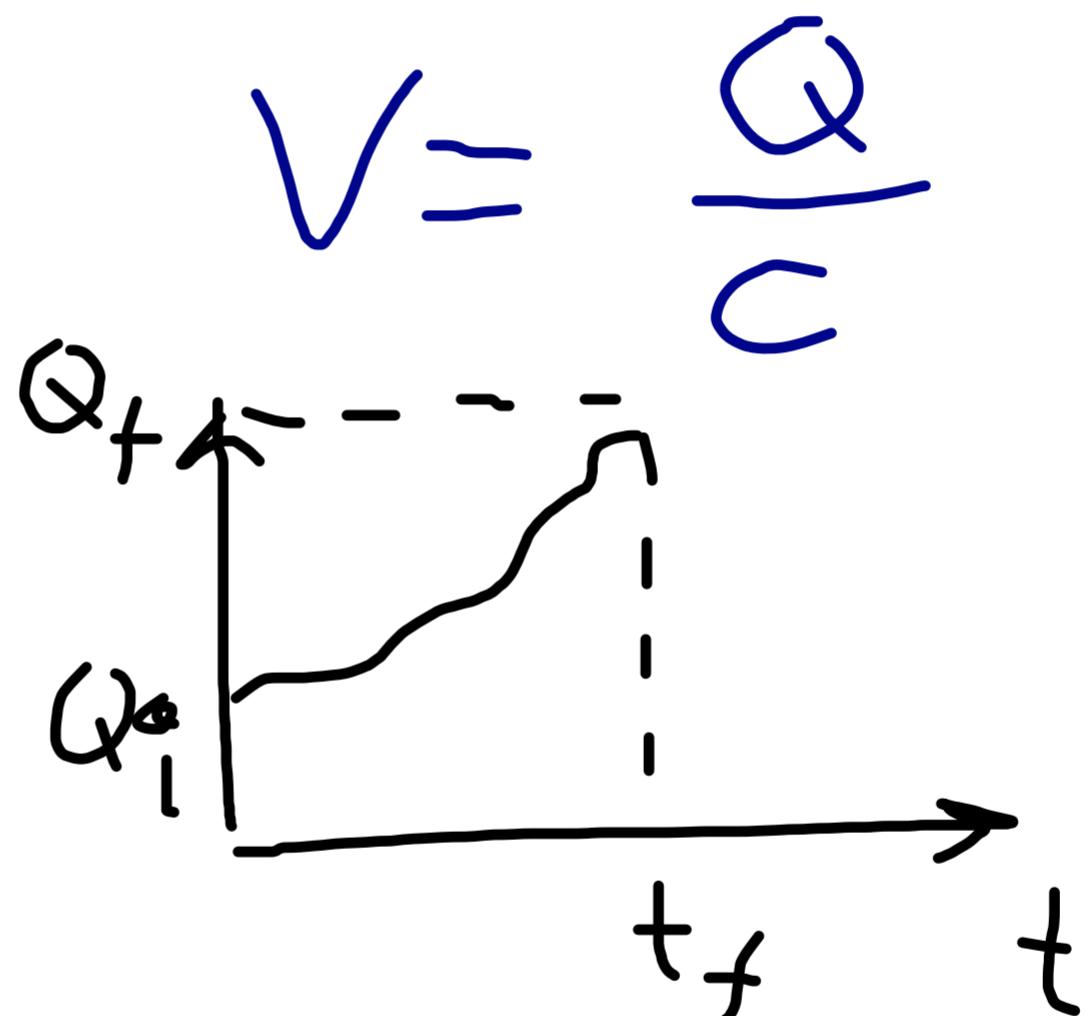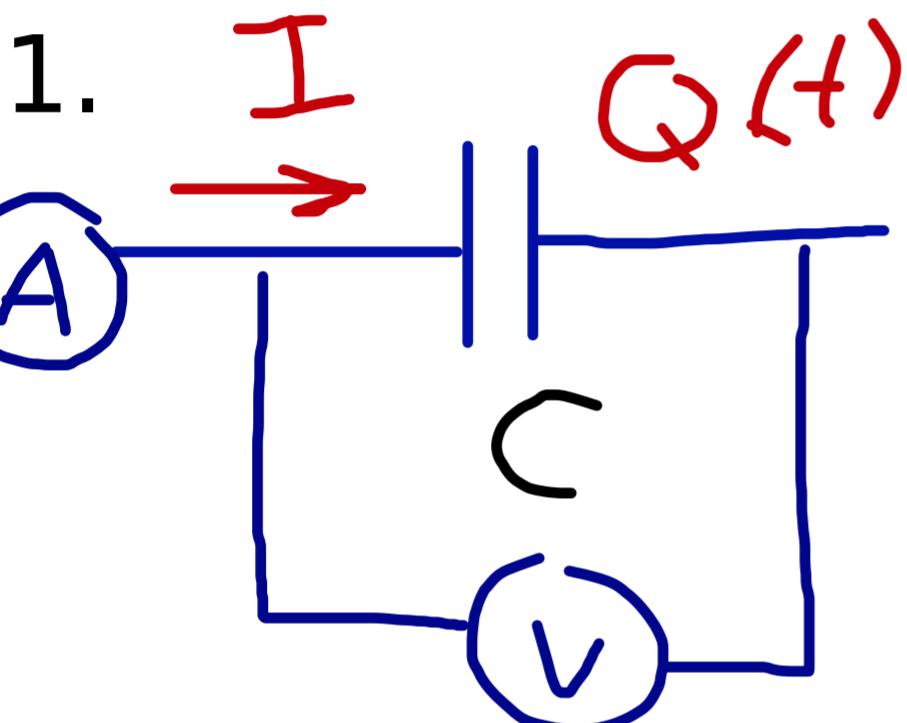1. Capacitor's energy. El. field energy
2. Capacitor and inductor in a circuit
3. RC and RL circuits
4. Energy dissipation
5. LC circuit



$$I = \frac{dQ}{dt}$$

$$P = IV = \frac{Q}{C} \frac{dQ}{dt}$$

$$dW = Pdt = \frac{1}{C} Q dQ$$


$$W = \int \frac{1}{C} Q dQ = \frac{Q_+^2}{2C} - \frac{Q_-^2}{2C}$$

$$E_c = \frac{Q^2}{2C}$$

Energy stored in a capacitor.


For a parallel plate capacitor
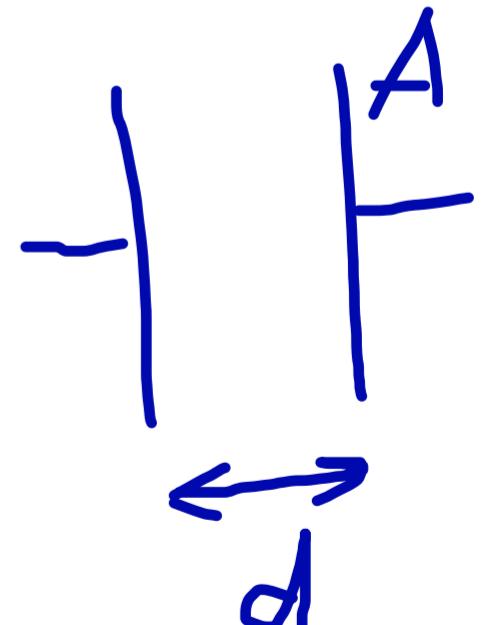
$$E = \frac{Q}{A\epsilon_0}; \quad C = \frac{A\epsilon_0}{d}$$




$$E_c = \frac{Q^2}{2\epsilon_0 A} \quad d = \frac{\epsilon_0 E^2}{2} A$$
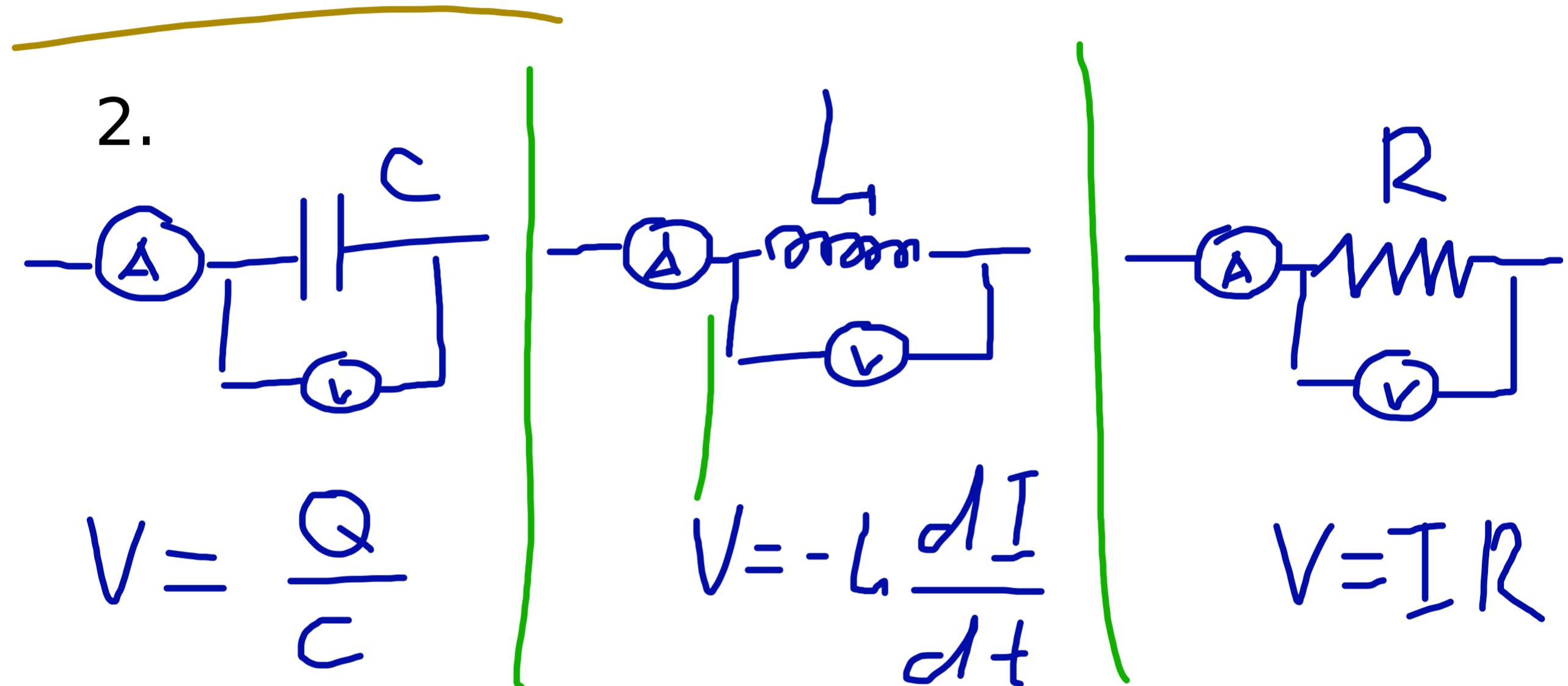
$$\mathcal{E}_E = \frac{\epsilon_0 E^2}{2}$$



$$I = \frac{dQ}{dt}$$

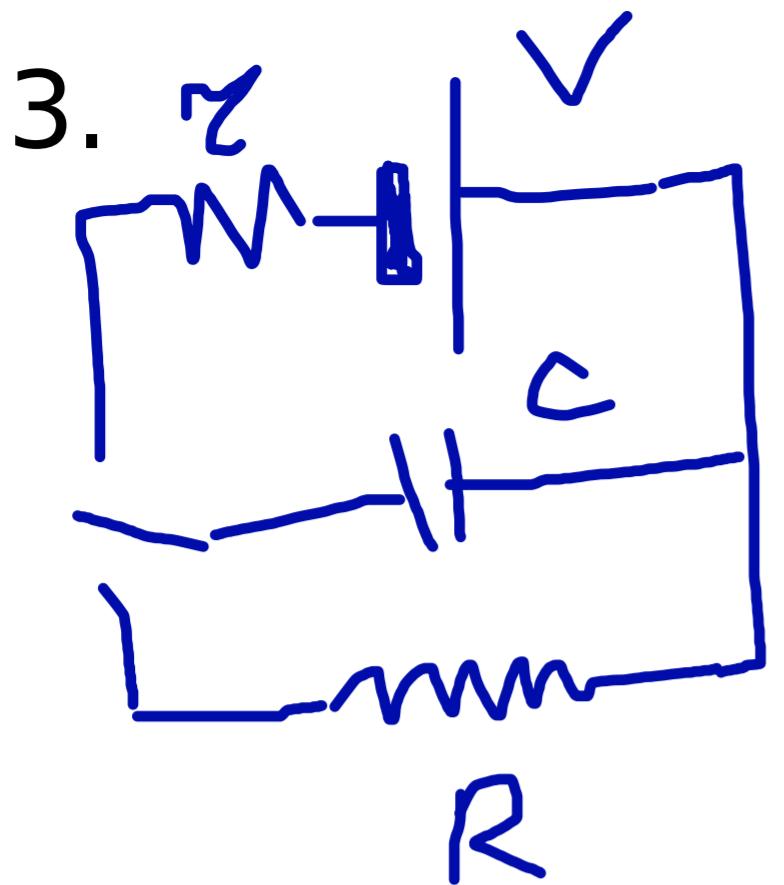

$$Q_0 = VC$$

$$t$$


$$\frac{Q}{C} + IR = D$$

$$I = \frac{1}{d+} \frac{Q}{dt}$$

$$\frac{d}{dt} E_r = -I^2 R$$


$$\frac{dQ}{dt} = -\frac{1}{RC} Q$$

$$Q = Q_0 e^{-t/\tau}$$

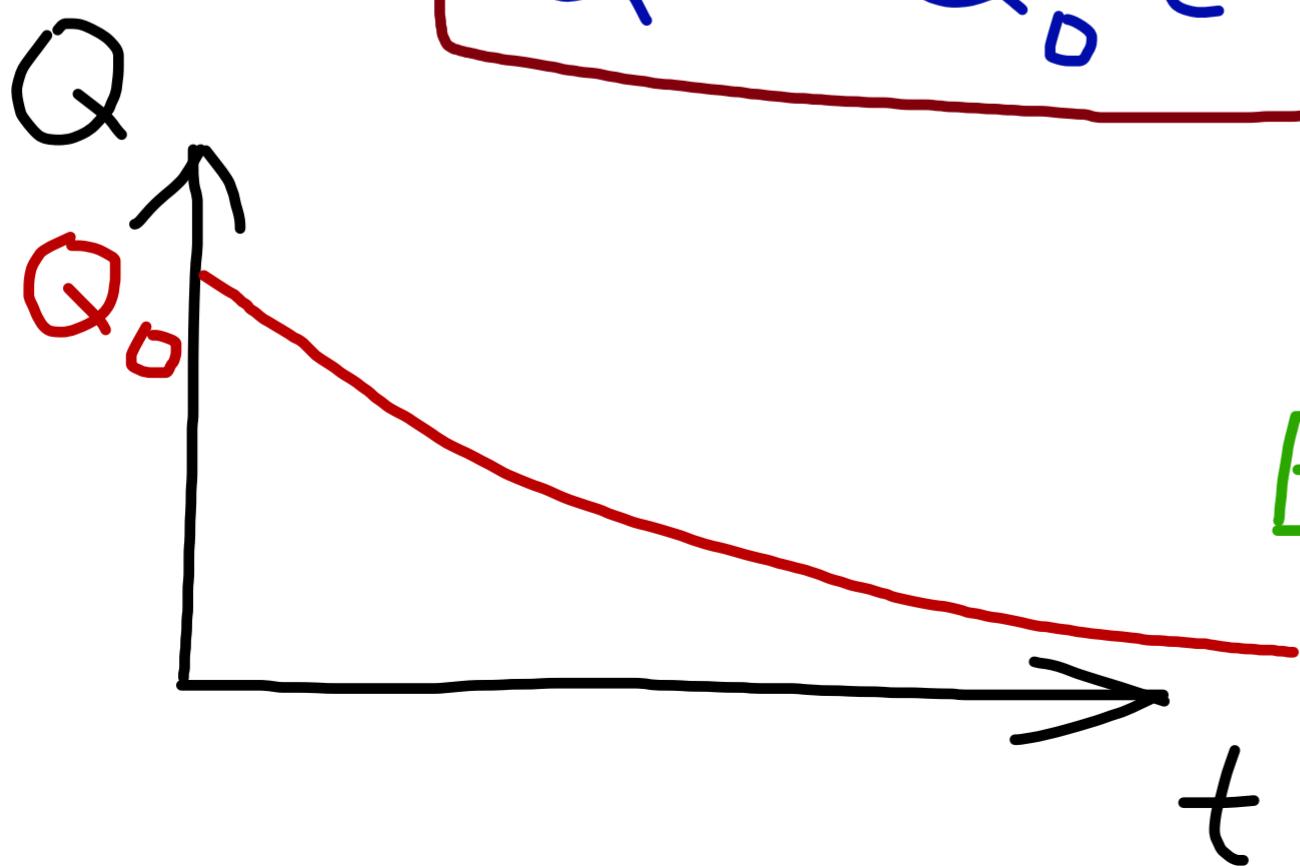

$$\tau = RC$$

$$E_r(t) = E_r e^{-2t/\tau}$$

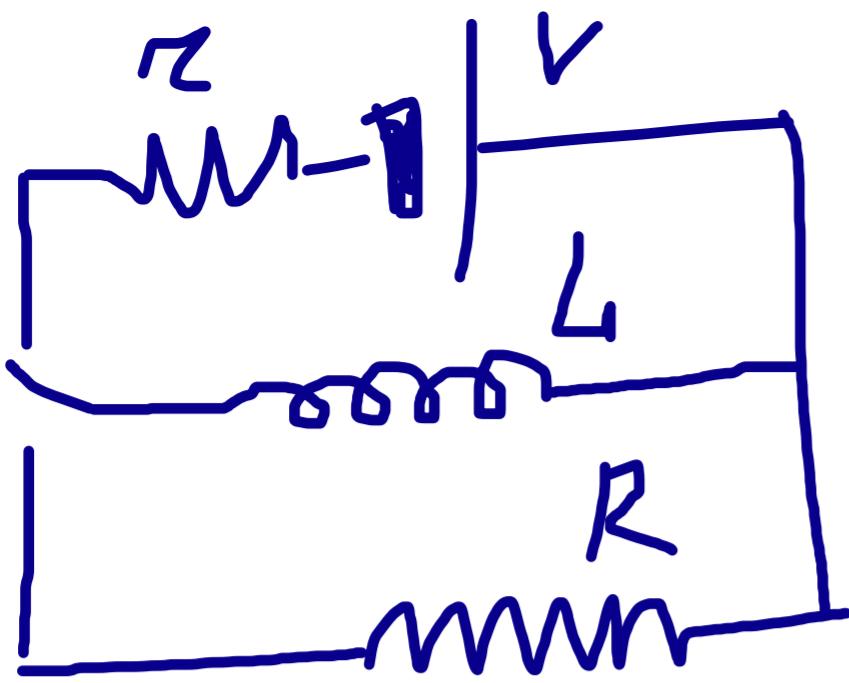

$$t = 0$$

$$I_0 = \frac{V}{R}$$

$t$

$$L \frac{dI}{dt} + RI = 0$$


$$I(t) = I_0 e^{-t/\tau}$$

$$\frac{1}{\tau} E_L = -RI^2$$

$$\tau = L/R$$

$$I_0 = \frac{V}{\tau}$$


$I$

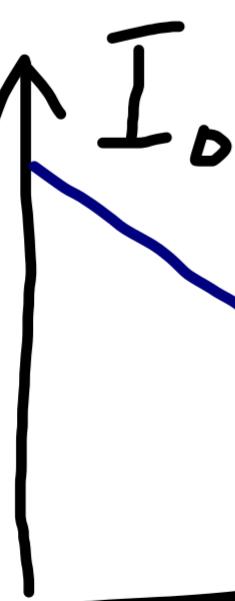

$$E_L(t) = E_0 e^{-2t/\tau}$$

$t$

# Charging

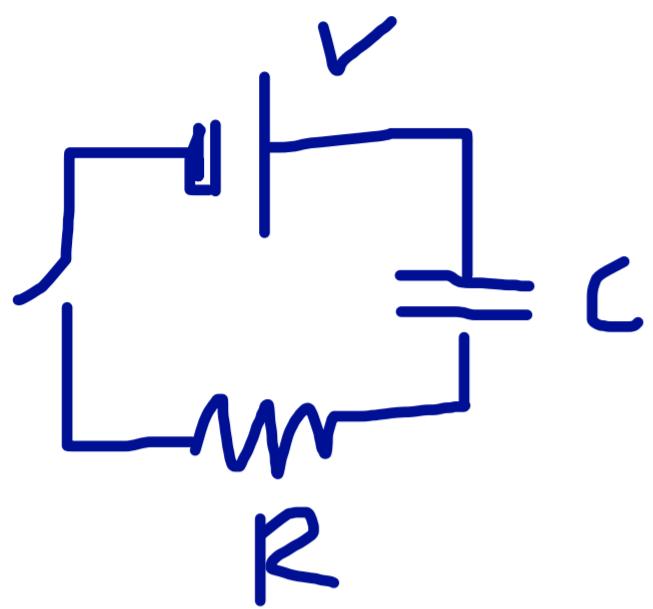


$$t = 0 \quad Q = 0$$

$$V - IR - \frac{Q}{C} = 0$$

$$Q = Q_+ (1 - e^{-t/\tau_C})$$

$$Q_+ = VC$$

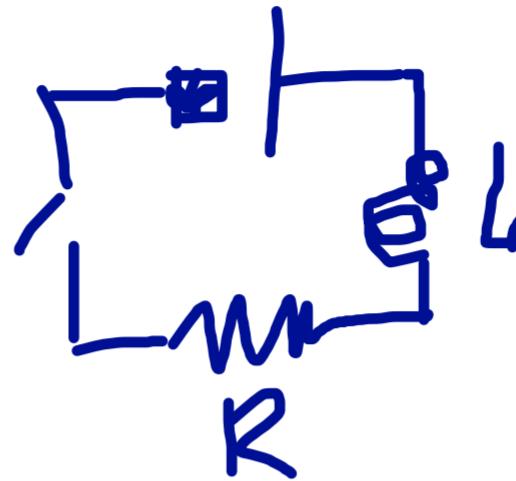


$$t = 0 \quad I = 0$$

$$V - IR - L \frac{dI}{dt} = 0$$

$$I = I_+ (1 - e^{-t/\tau_L})$$

$$I_+ = \frac{V}{R}$$

# lc circuit

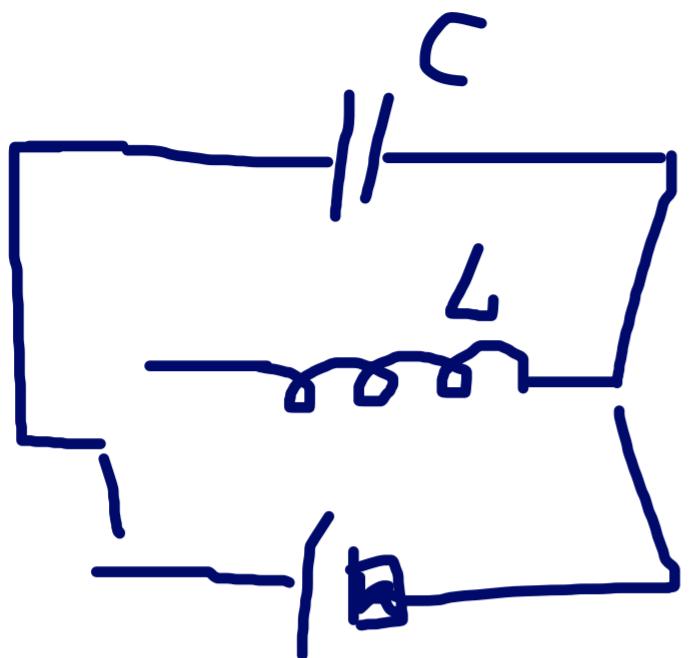

$$t = 0$$

$$I = 0$$

$$\underline{Q_0 = CV}$$

V

$$t = 0 \quad -V_C + V_L = 0$$

$$\frac{Q}{C} + L \frac{dI}{dt} = 0$$



$$I = \frac{dQ}{dt}$$

$$\frac{d}{dt} (E_C + E_L) = 0$$

$$\frac{d^2Q}{dt^2} = -\frac{1}{LC} Q \quad | \quad Q = Q_0 \cos(\omega t)$$

$$\omega = 1/\sqrt{LC}$$

## RLC circuit

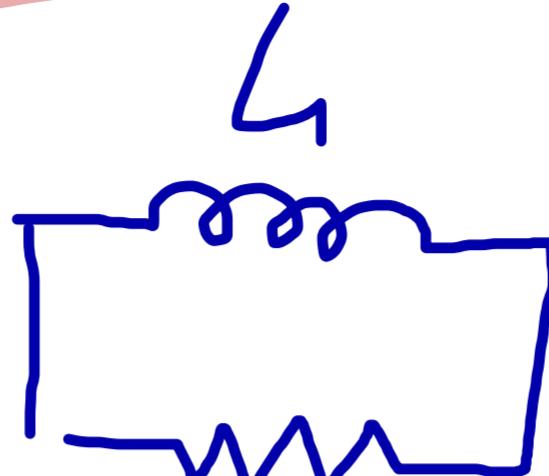
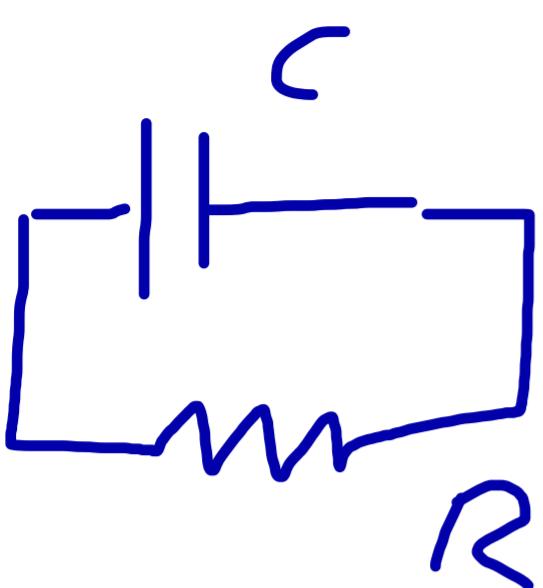


$$Q = Q_0 e^{-t/\tau}$$



$$I = I_0 e^{-t/\tau}$$

$$\tau = RC$$

$$\tau = L/R$$

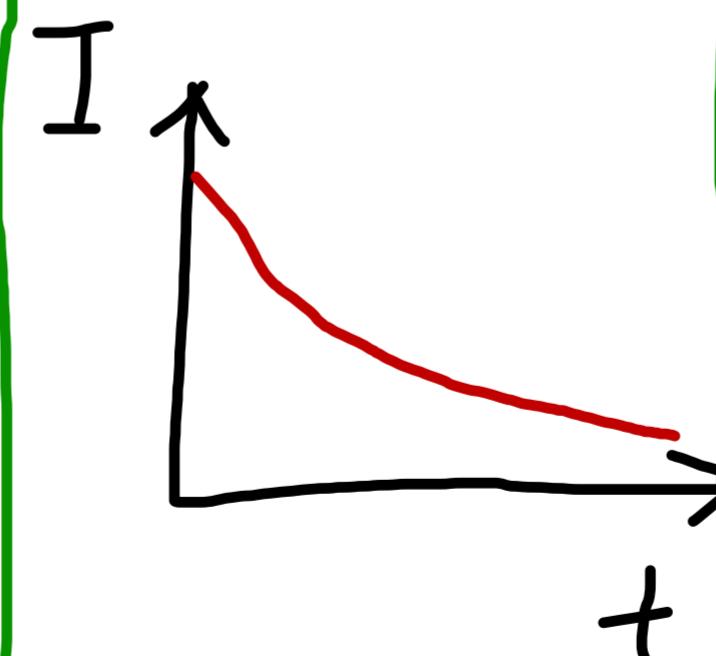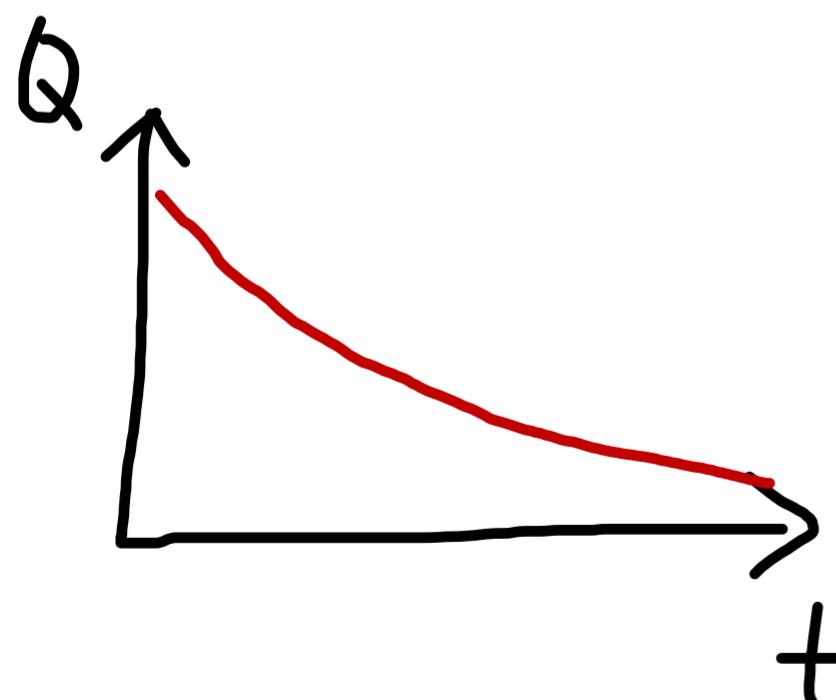

$$\omega_0^2 = 1/LC$$

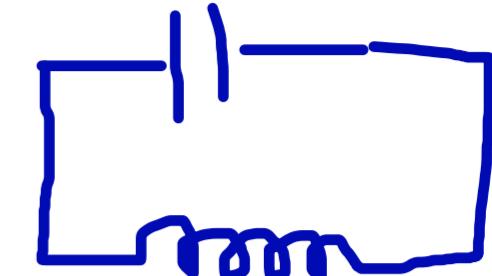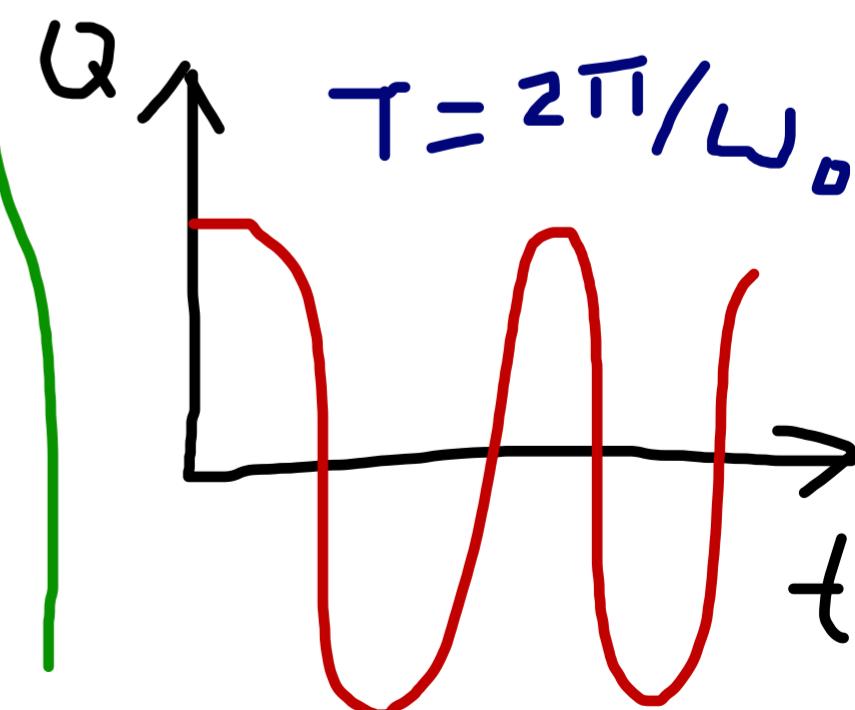


$$Q(t=0) = Q_0$$

$$Q = Q_0 \cos(\omega_0 t)$$

$$I = -\omega_0 Q_0 \sin(\omega_0 t)$$

$$\omega_0^2 = 1/LC$$

$$\tau = 2\pi/\omega_0$$

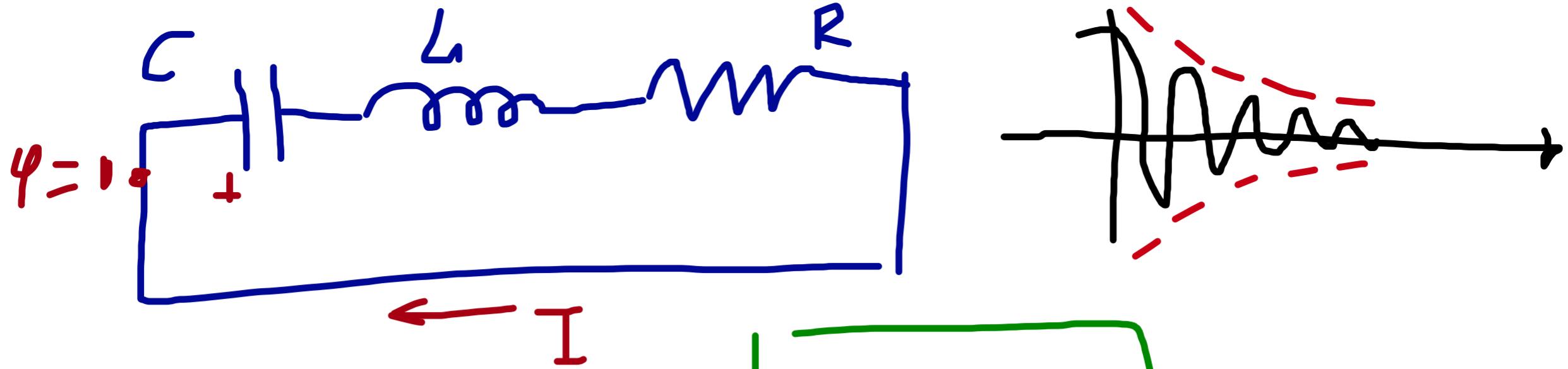

$$V_C + V_L + V_R = 0$$

$$I = \frac{dQ}{dt}$$

$$-\frac{Q}{C} - \zeta \frac{dI}{dt} - RI = 0$$

$$L \frac{d^2Q}{dt^2} + R \frac{dQ}{dt} + \frac{1}{C} Q = 0$$

$$Q(t) = Q_0 e^{-t/\tau} \cos(\omega t)$$

$$\tau = 2L/R$$

$$\omega^2 = \frac{1}{LC} - \frac{1}{\tau^2}$$

## Plan

1. Exam discussion
2. Driven oscillator

Count: 83

Ave: 44.8

Std: 19.4

Max: 91

$100 > A > 64$

$64 > B > 14$



$44 > C > 24$

$24 > D > 10$

---

Solutions of the Exam  
Problems

## 2. Driven Oscillator

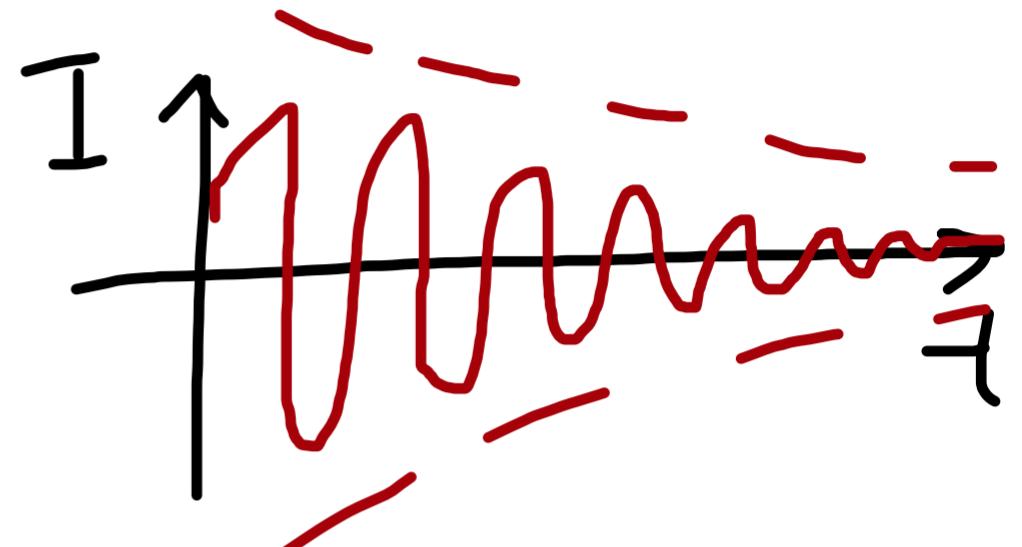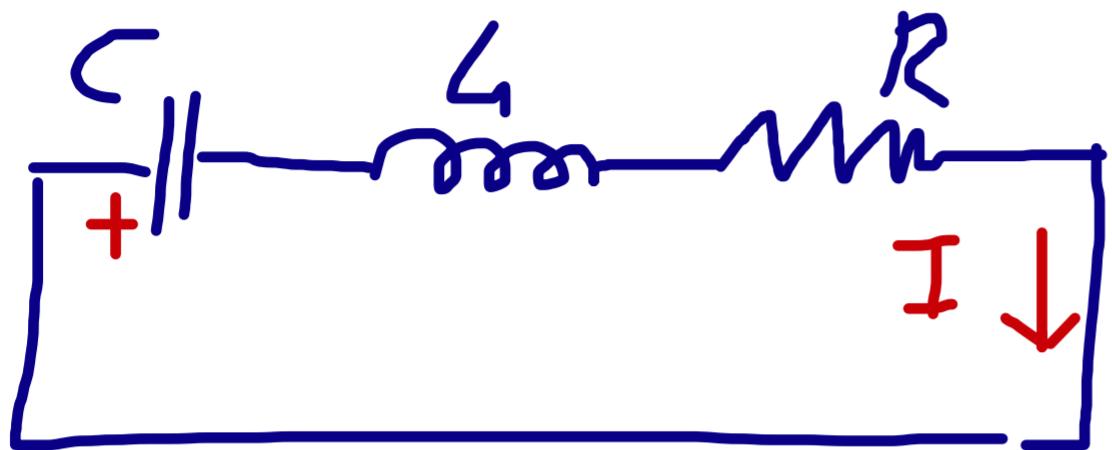

$$I = \frac{dQ}{dt} \quad -\frac{Q}{C} - L \frac{dI}{dt} - RI = 0$$


$$Q_o(t) = A e^{-t/\tau} \cos(\omega_o t + \varphi)$$

$$\tau = \frac{2L}{R}$$


$$; \quad \omega_o^2 = \frac{1}{LC} - \frac{1}{\tau^2}$$

independent of  
init. cond.
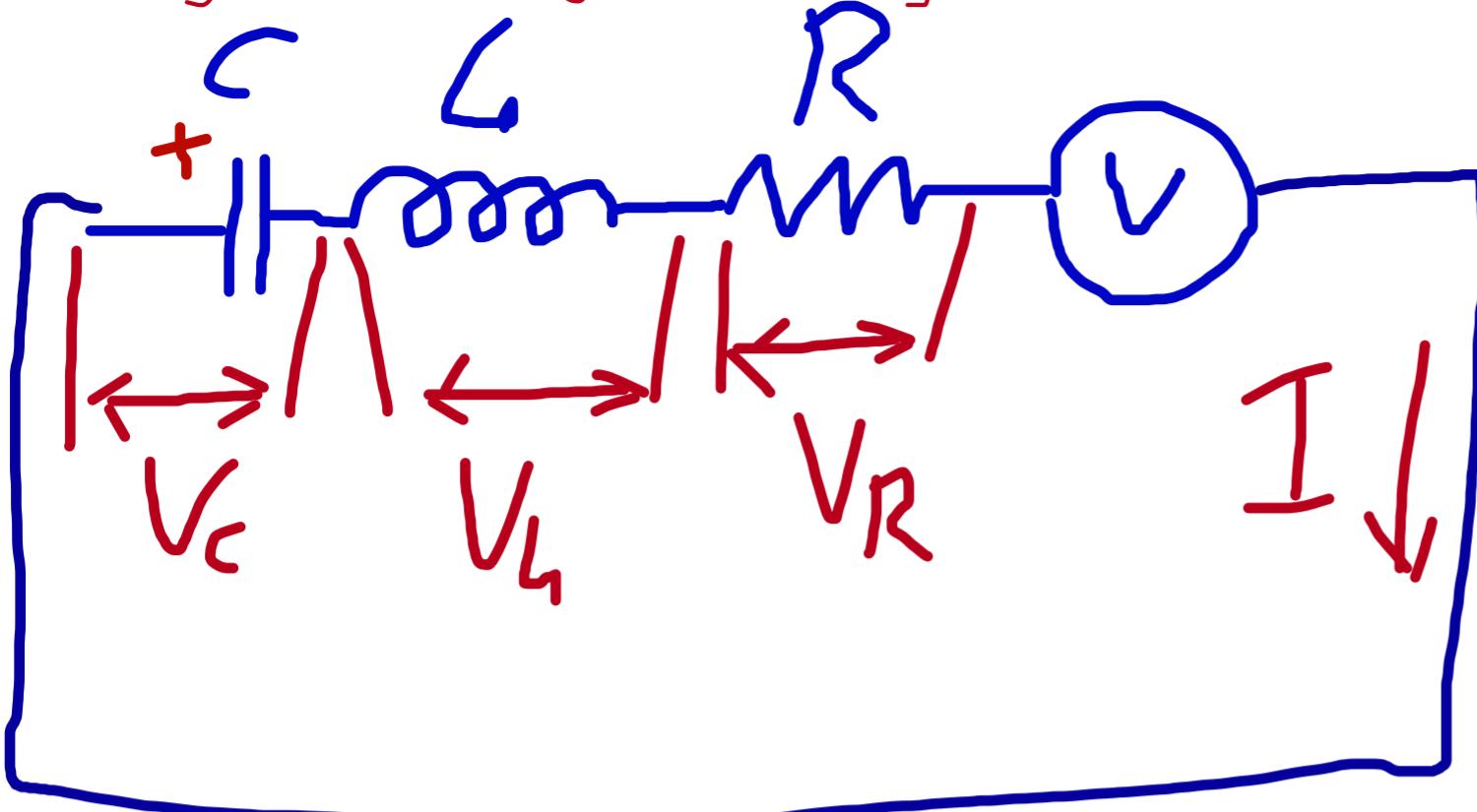
$$\cos(\omega t + \phi) = \cos \omega t \cos \phi - \sin \omega t \sin \phi$$



$$V = V_0 \cos(\omega t)$$

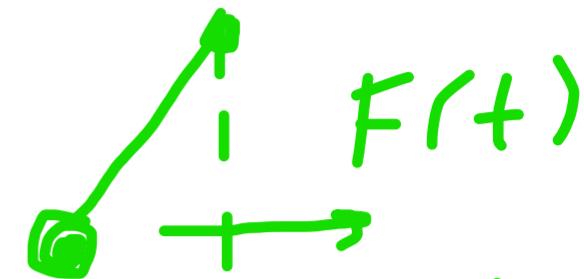

$$I = \frac{dQ}{dt}$$

Phase shift

$$-\frac{Q}{C} - L \frac{dI}{dt} - IR = V(t)$$

solution  
↙

$$Q(t) + Q_0(t)$$

also solution!

Decays  
(Takes care  
of init. cond)

Non Decaying  
solution!

$$-\frac{Q}{C} - L \frac{dI}{dt} - IR = V(t) \quad \left| \begin{array}{l} I = \frac{dQ}{dt} \\ \hline \end{array} \right.$$

$$Q = Q_m \cos(\omega t + \theta)$$

$\approx L(\omega^2 - \omega_0^2)$

$$\left( -\frac{1}{C} + \omega^2 L \right) Q_m \cos(\omega t + \theta) +$$

$$+ \omega R \theta_m \sin(\omega t + \theta) = V_0 \cos(\omega t + \theta - \theta) =$$

$$= V_0 \cos(\omega t + \theta) \cos \theta +$$

$$+ V_0 \sin(\omega t + \theta) \sin \theta$$

$$\omega R Q_m = V_0 \sin \theta$$

$$L(\omega^2 - \omega_0^2) Q_m = V_0 \cos \theta$$

$$\tan \theta = \frac{\omega R}{L(\omega^2 - \omega_0^2)}$$


$$Q_m = \frac{V_b}{[\omega^2 R^2 + L^2 (\omega^2 - \omega_0^2)^2]^{1/2}}$$

$$I = -Q_m \omega \cos(\omega t + \theta)$$

Power  $R$

$$\bar{P} = \bar{I}V$$


$$\bar{P}_L = \bar{P}_c = 0$$

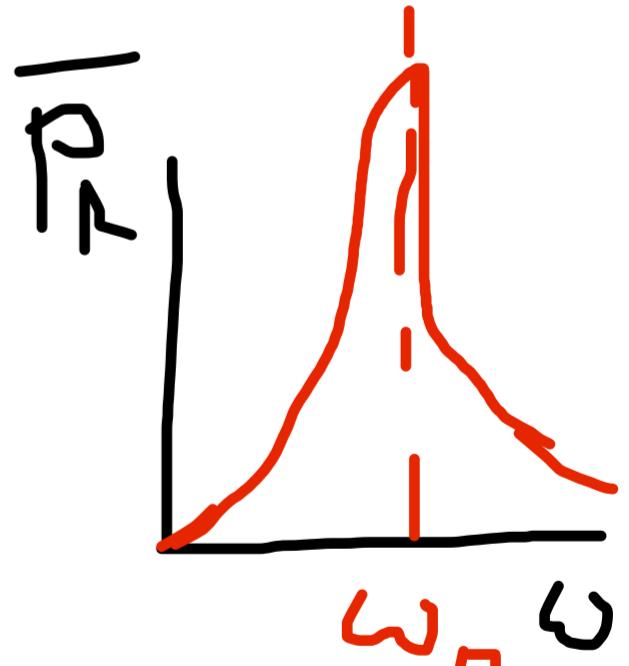

$$\bar{P}_R = \frac{R \bar{I}_m^2}{2} = \frac{R \omega^2 V_b^2}{2} \frac{1}{\omega^2 R^2 + L^2 (\omega^2 - \omega_0^2)^2}$$


$$\omega_R^2 = \frac{1}{Lc} - \frac{2}{\tau^2}$$

# Maxwell's equations

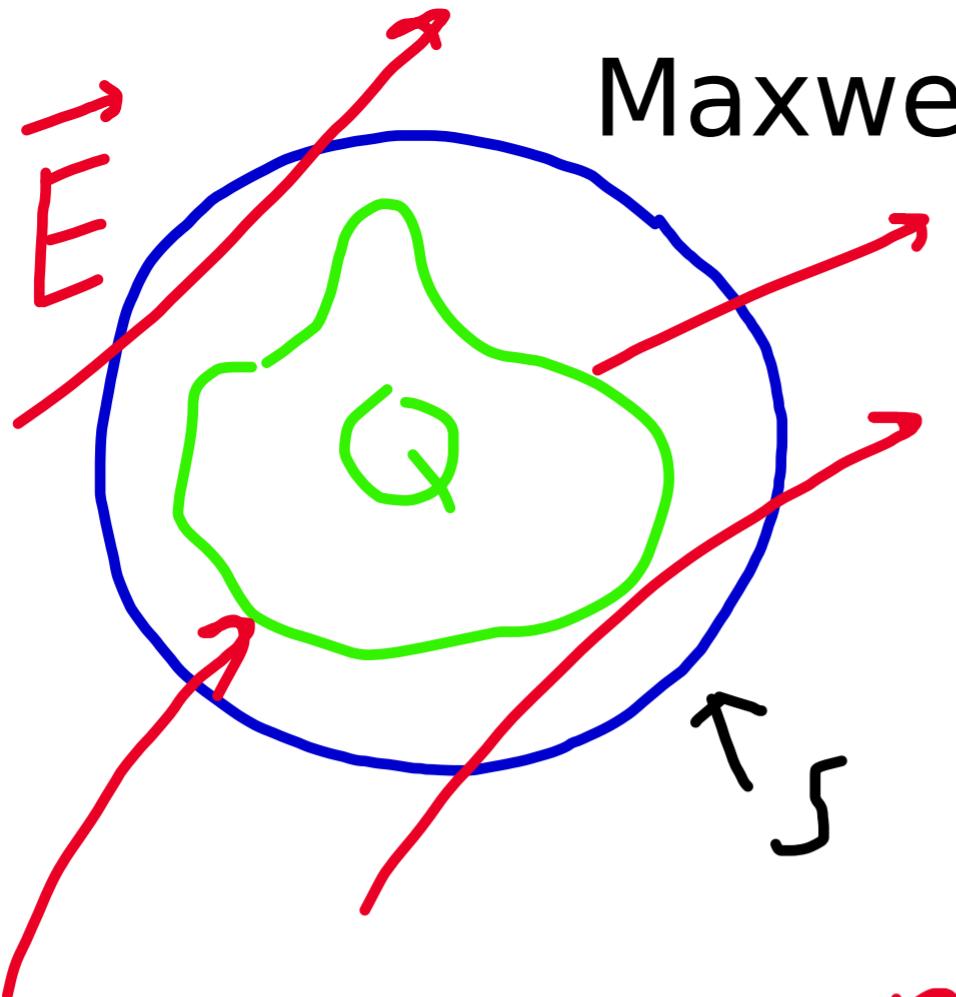


$$\oint_S \vec{E} \cdot d\vec{A} = Q/\epsilon_0$$

Gauss's law

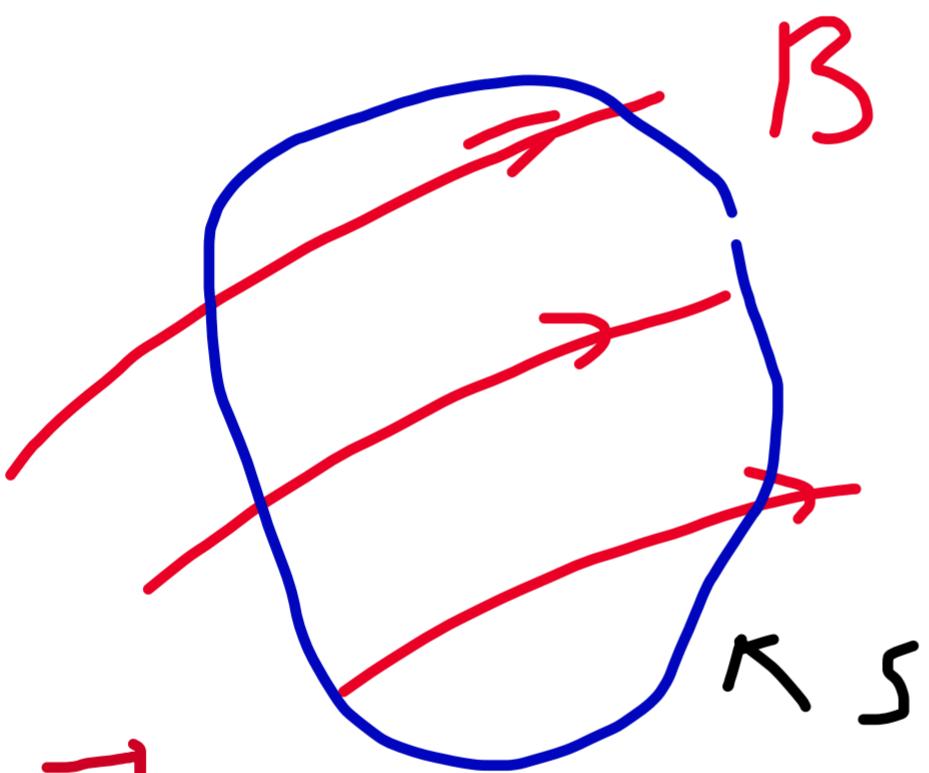


$$\oint_S \vec{B} \cdot d\vec{A} = 0$$

Faraday's law

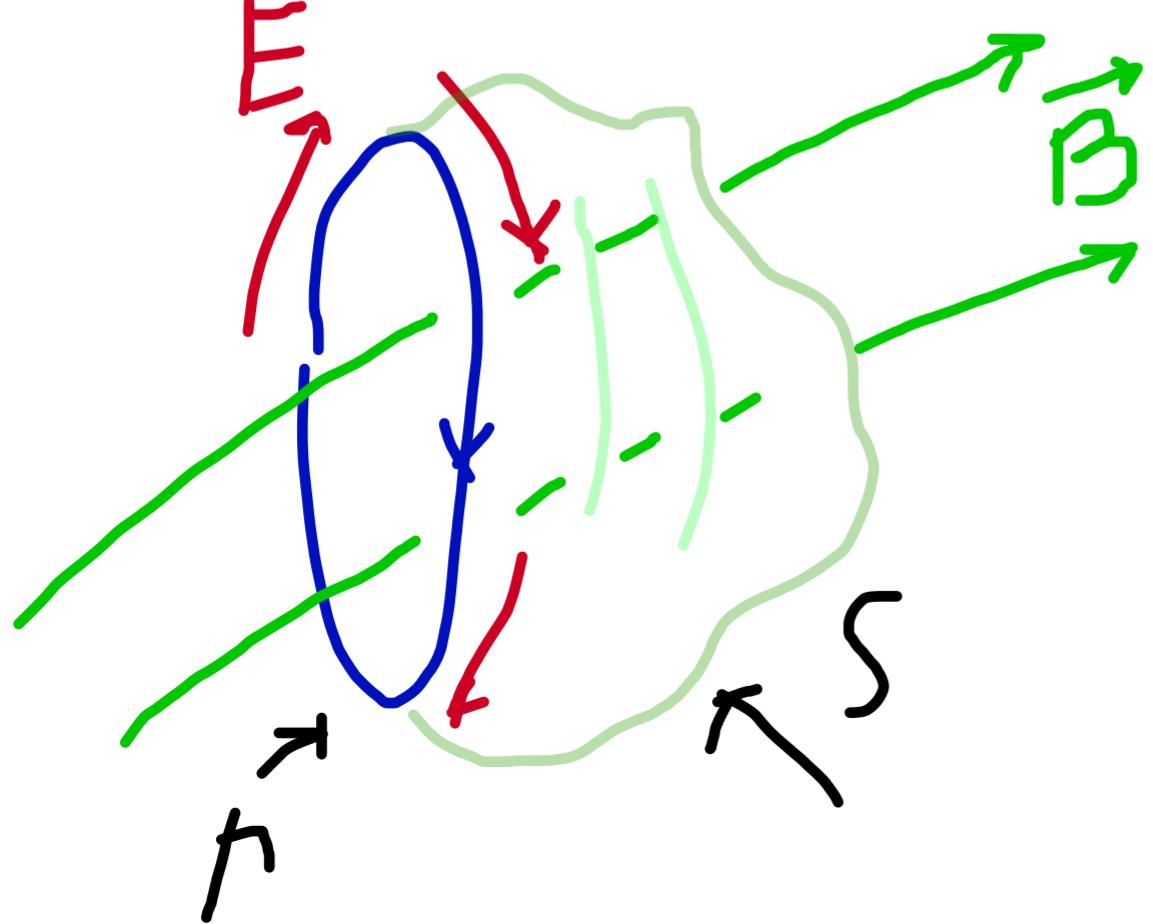
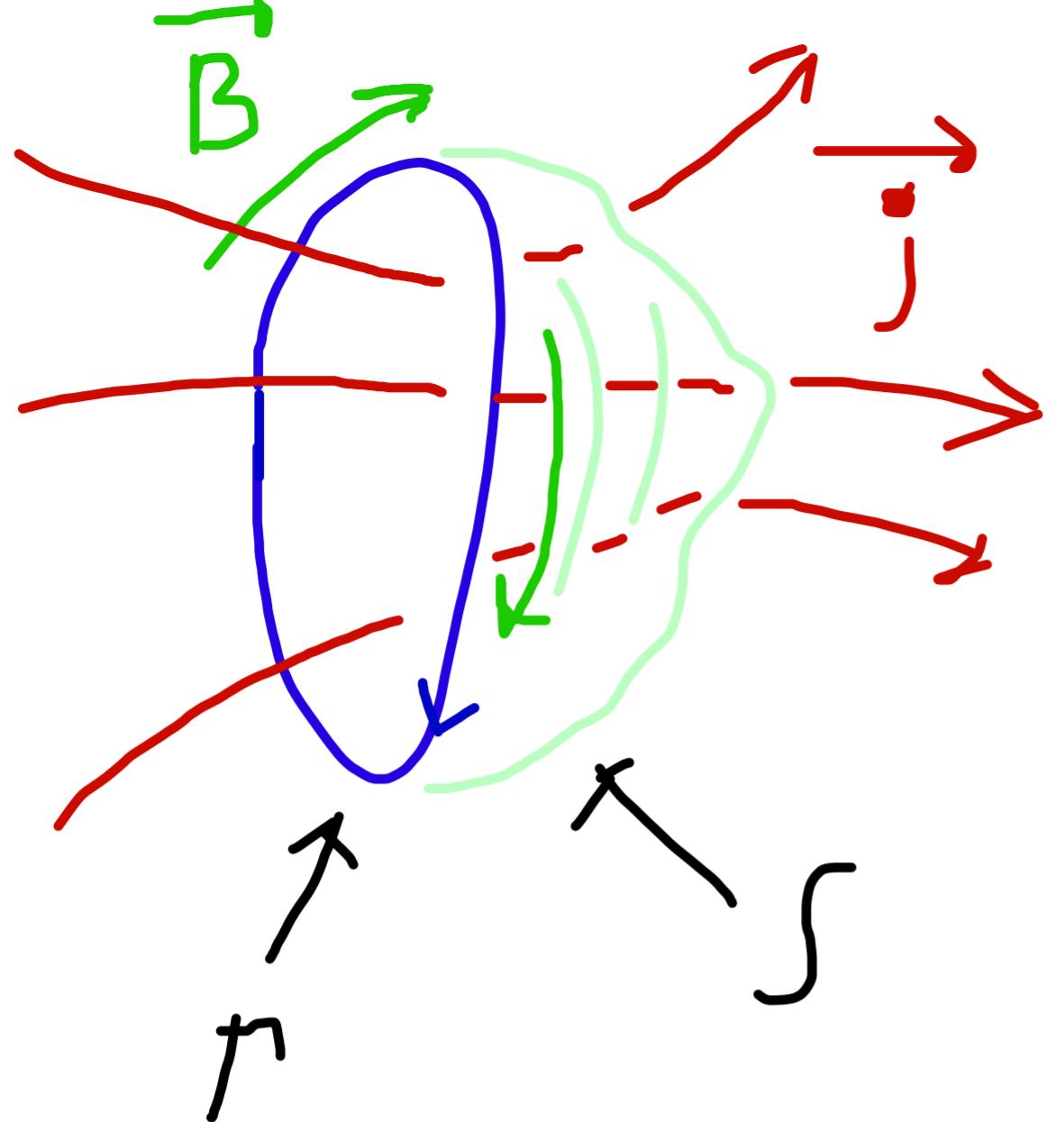
$$\oint_C \vec{E} \cdot d\vec{l} = -\frac{1}{\mu_0} \int_S \vec{B} \cdot d\vec{A}$$




$$\oint \vec{B} \cdot d\vec{l} = \mu_0 \int \vec{j} \cdot d\vec{A}$$

$\int \limits_{\mathcal{P}}$        $\int \limits_{\mathcal{S}}$

Ampere's law

$$\mu_0 \int \vec{E} \cdot d\vec{l} =$$

Something is not  
right

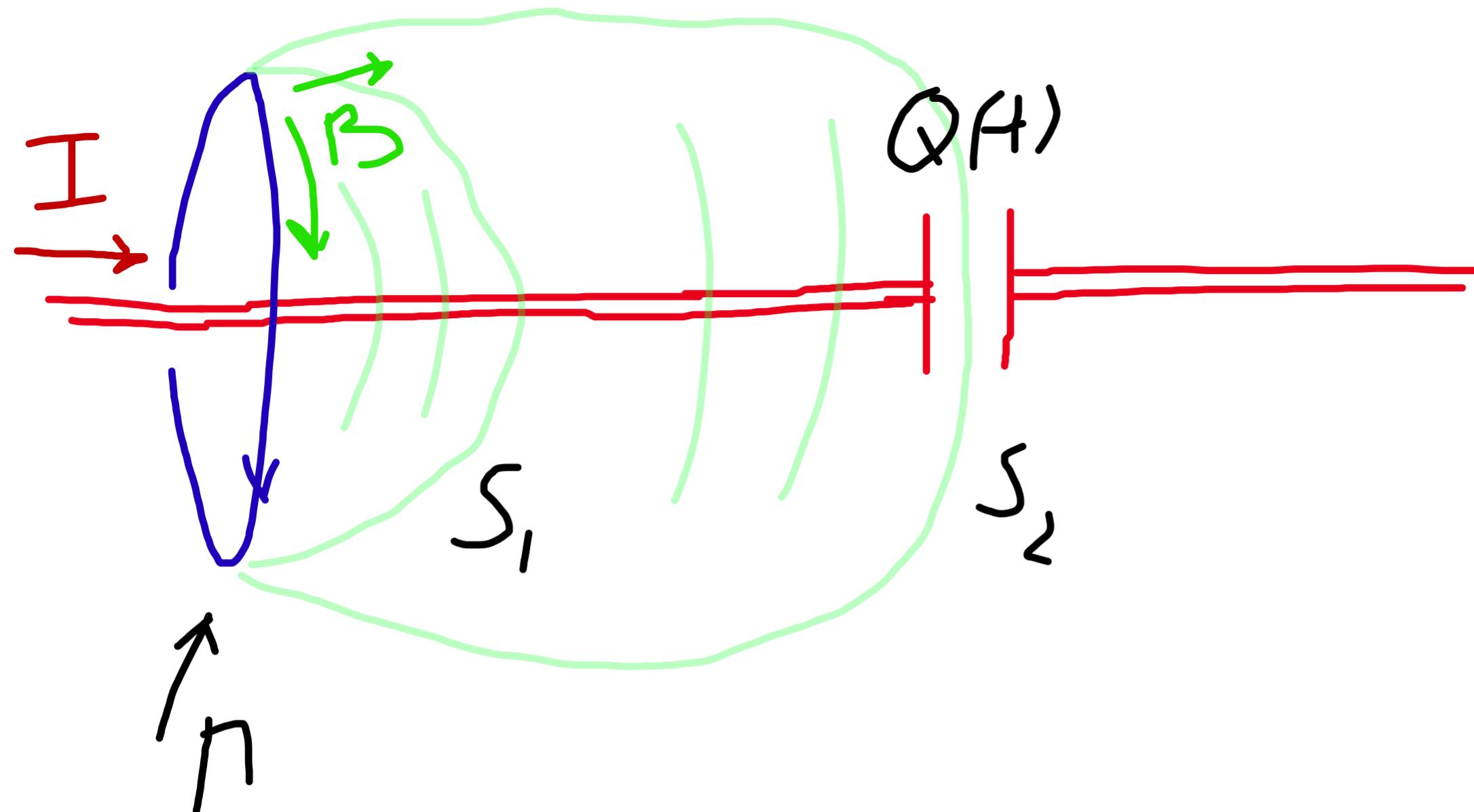


use  $S_1$ :

$$\oint \vec{B} \cdot d\vec{l} = \mu_0 I$$

use  $S_2$ :

$$\oint \vec{B} \cdot d\vec{l} = ?$$

no current through  $S_2$

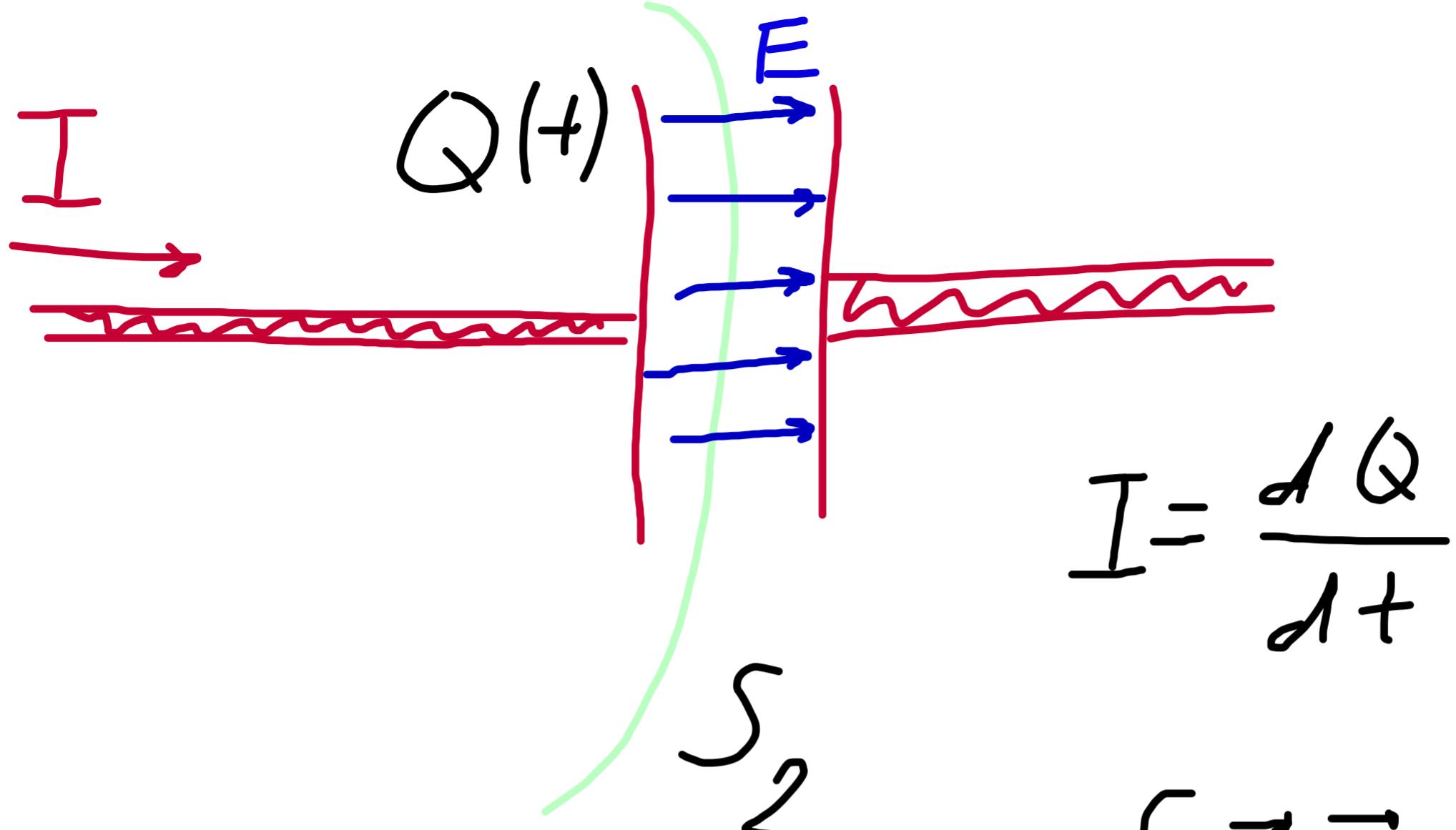

Gauss

$$\int_{S_2} \vec{E} \cdot d\vec{A} = \frac{Q}{\epsilon_0}$$

$$I = \epsilon_0 \frac{d}{dt} \int_{S_2} \vec{E} \cdot d\vec{A}$$

$$\oint_{P} \vec{B} \cdot d\vec{l} = \mu_0 \epsilon_0 \frac{d}{dt} \int_S \vec{E} \cdot d\vec{A} + \mu_0 \int_S \vec{j} \cdot d\vec{A}$$

In empty space

$$\oint \vec{E} \cdot d\vec{A} = 0 + Q/\epsilon_0$$

$$\oint \vec{B} \cdot d\vec{A} = 0$$

$$\oint \vec{E} \cdot d\vec{l} = -\frac{d}{dt} \int \vec{B} \cdot d\vec{A}$$

$$\oint \vec{B} \cdot d\vec{l} = \epsilon_0 \mu_0 \frac{d}{dt} \int \vec{E} \cdot d\vec{A} + \mu_0 \int \vec{j} \cdot d\vec{A}$$

multiserial Eq.  $\vec{j} = \sigma \vec{E}$